 

DIGITAL DESIGN
THIRD EDITION



Digital Design 3e, Morris Mano

Chapter 4 – Combinational Logic

MODULAR DESIGN OF COMBINATIONAL CIRCUITS


Circuit Analysis Procedure

Overview

- **Important concept – analyze digital circuits**
 - **Given a circuit**
 - Create a truth table
 - Create a minimized circuit
- **Approaches**
 - **Boolean expression approach**
 - **Truth table approach**
- **Leads to minimized hardware**
- **Provides insights on how to design hardware**
 - **Tie in with K-maps (next time)**


The Problem

 - How can we convert from a circuit drawing to an equation or truth table?
- Two approaches
 - Create intermediate equations
 - Create intermediate truth tables




Label Gate Outputs

1. Label all gate outputs that are a function of input variables.
2. Label gates that are a function of input variables and previously labeled gates.
3. Repeat process until all outputs are labelled.

 


Approach 1: Create Intermediate Equations

- ❑ Step 1: Create an equation for each gate output based on its input.
- $R = ABC$
 - $S = A + B$
 - $T = C'S$
 - $Out = R + T$

 


Approach 1: Substitute in subexpressions

- ❑ Step 2: Form a relationship based on input variables (A, B, C)
 - $R = ABC$
 - $S = A + B$
 - $T = C'S = C'(A + B)$
 - $\text{Out} = R + T = ABC + C'(A + B)$

 

Approach 1: Substitute in subexpressions


- ❑ Step 3: Expand equation to SOP final result
 - **Out = $ABC + C'(A+B) = ABC + AC' + BC'$**

 

Approach 2: Truth Table

- Step 1: Determine outputs for functions of input variables.

A	B	C	R	S
0	0	0	0	0
0	0	1	0	0
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


Approach 2: Truth Table

- Step 2: Determine outputs for functions of intermediate variables.

$$T = S * C'$$

A	B	C	C'	R	S	T
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	1	1
0	1	1	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	0	1	0
1	1	0	1	0	1	1
1	1	1	0	1	1	0

 


Approach 2: Truth Table

- Step 3: Determine outputs for function.

$$R + T = \text{Out}$$

A	B	C	R	S	T	Out
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	1	1	1
0	1	1	0	1	0	0
1	0	0	0	1	1	1
1	0	1	0	1	0	0
1	1	0	0	1	1	1
1	1	1	1	1	0	1

 

More Difficult Example

□ Step 3: Note labels on interior nodes

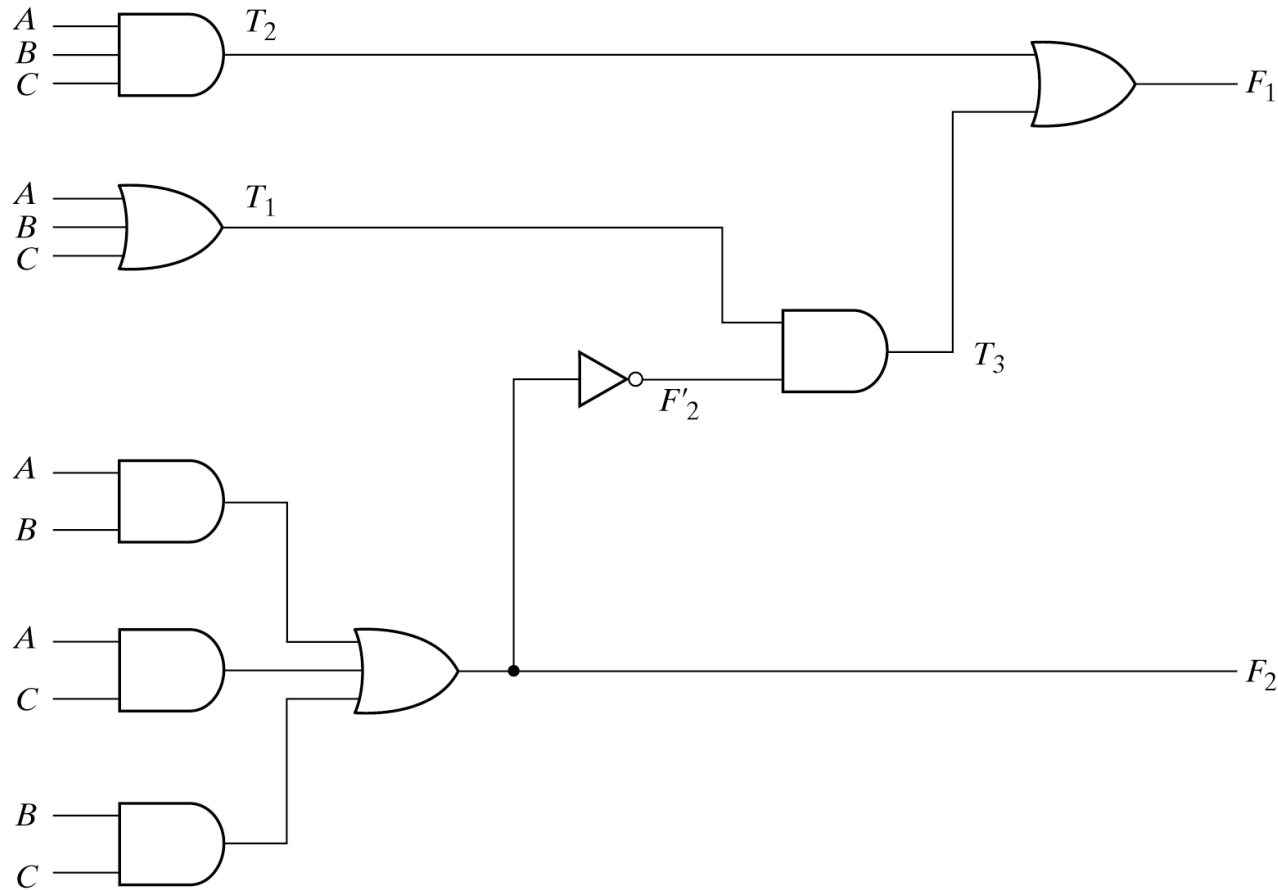


Fig. 4-2 Logic Diagram for Analysis Example

More Difficult Example: Truth Table

- ❑ Remember to determine intermediate variables starting from the inputs.
- ❑ When all inputs determined for a gate, determine output.
- ❑ The truth table can be reduced using K-maps.

A	B	C	F_2	F'_2	T_1	T_2	T_3	F_1
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

Summary

- Important to be able to convert circuits into truth table and equation form
 - **WHY? ---- leads to minimized sum of product representation**
- Two approaches illustrated
 - **Approach 1: Create an equation with circuit output dependent on circuit inputs**
 - **Approach 2: Create a truth table which shows relationship between circuit inputs and circuit outputs**
- Both results can then be minimized using K-maps.
- Next time: develop a minimized SOP representation from a high level description

Combinational Design Procedure

Overview

- Design digital circuit from specification
- Digital inputs and outputs known
 - Need to determine logic that can *transform* data
- Start in truth table form
- Create K-map for each output based on function of inputs
- Determine minimized sum-of-product representation
- Draw circuit diagram

Design Procedure (Mano)

Design a circuit from a specification.

1. Determine number of required inputs and outputs.
2. Derive truth table
3. Obtain simplified Boolean functions
4. Draw logic diagram and verify correctness

$$S = A + B + C$$
$$R = ABC$$

A	B	C	R	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Previously, we have learned...

- **Boolean algebra can be used to simplify expressions, but not obvious:**
 - **how to proceed at each step, or**
 - **if solution reached is minimal.**
- **Have seen five ways to represent a function:**
 - **Boolean expression**
 - **truth table**
 - **logic circuit**
 - **minterms/maxterms**
 - **Karnaugh map**


Combinational logic design

- **Use multiple representations of logic functions**
- **Use graphical representation to assist in simplification of function.**
- **Use concept of “don’t care” conditions.**
- **Example - encoding BCD to seven segment display.**
- **Similar to approach used by designers in the field.**

BCD to Seven Segment Display

- Used to display binary coded decimal (BCD) numbers using seven illuminated segments.
- BCD uses 0's and 1's to represent decimal digits 0 - 9. Need four bits to represent required 10 digits.
- Binary coded decimal (BCD) represents each decimal digit with four bits


0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
.
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

 

BCD to seven segment display

- ° List the segments that should be illuminated for each digit.

0	a,b,c,d,e,f
1	b,c
2	a,b,d,e,g
3	a,b,c,d,g
4	b,c,f,g
5	a,c,d,f,g
6	a,c,d,e,f,g
7	a,b,c
8	a,b,c,d,e,f,g
9	a,b,c,d,f,g

 

BCD to seven segment display

- ° Derive the truth table for the circuit.
- ° Each output column in one circuit.

	Inputs				Outputs					
Dec	w	x	y	z	a	b	c	d	e	.
0	0	0	0	0	1	1	1	1	1	.
1	0	0	0	1	0	1	1	0	0	.
2	0	0	1	0	1	1	0	1	1	.
.
7	0	1	1	1	1	1	1	0	0	.
8	1	0	0	0	1	1	1	1	1	.
9	1	0	0	1	1	1	1	1	0	.

BCD to seven segment display

- Find minimal sum-of-products representation for each **output**

For segment “a” :

wx \ yz	yz			
	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11				
10	1	1		

Note: Have only filled in ten squares, corresponding to the ten numerical digits we wish to represent.

Don't care conditions (BCD display) ...

- Fill in don't cares for **undefined** outputs.
 - Note that these combinations of inputs should never happen.
- Leads to a reduced implementation

For segment “a” :

		yz			
		00	01	11	10
wx	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X

Put in “X” (don't care), and interpret as either 1 or 0 as desired

Don't care conditions (BCD display) ...

- Circle biggest group of 1's and Don't Cares.
- Leads to a reduced implementation

For segment “a” :

		yz			
		00	01	11	10
wx	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X

$$F_{a1} = y$$

Don't care conditions (BCD display)

- Circle biggest group of 1's and Don't Cares.
- Leads to a reduced implementation

For segment “a” :

wx \ yz	yz			
	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	X	X	X	X
10	1	1	X	X

$$F_{a2} = w$$

Don't care conditions (BCD display) ...

- Circle biggest group of 1's and Don't Cares.
- All 1's should be covered by at least one implicant

For segment “a” :

		yz			
		00	01	11	10
wx	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X

$$F_{a3} = \bar{x}\bar{z}$$

		yz			
		00	01	11	10
wx	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X

$$F_{a4} = xz$$

Don't care conditions (BCD display) ...


- Put all the terms together
- Generate the circuit

For segment “a” :

		yz			
		00	01	11	10
wx	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X

$$F = y + w + \overline{\overline{x}}\overline{\overline{z}} + xz$$

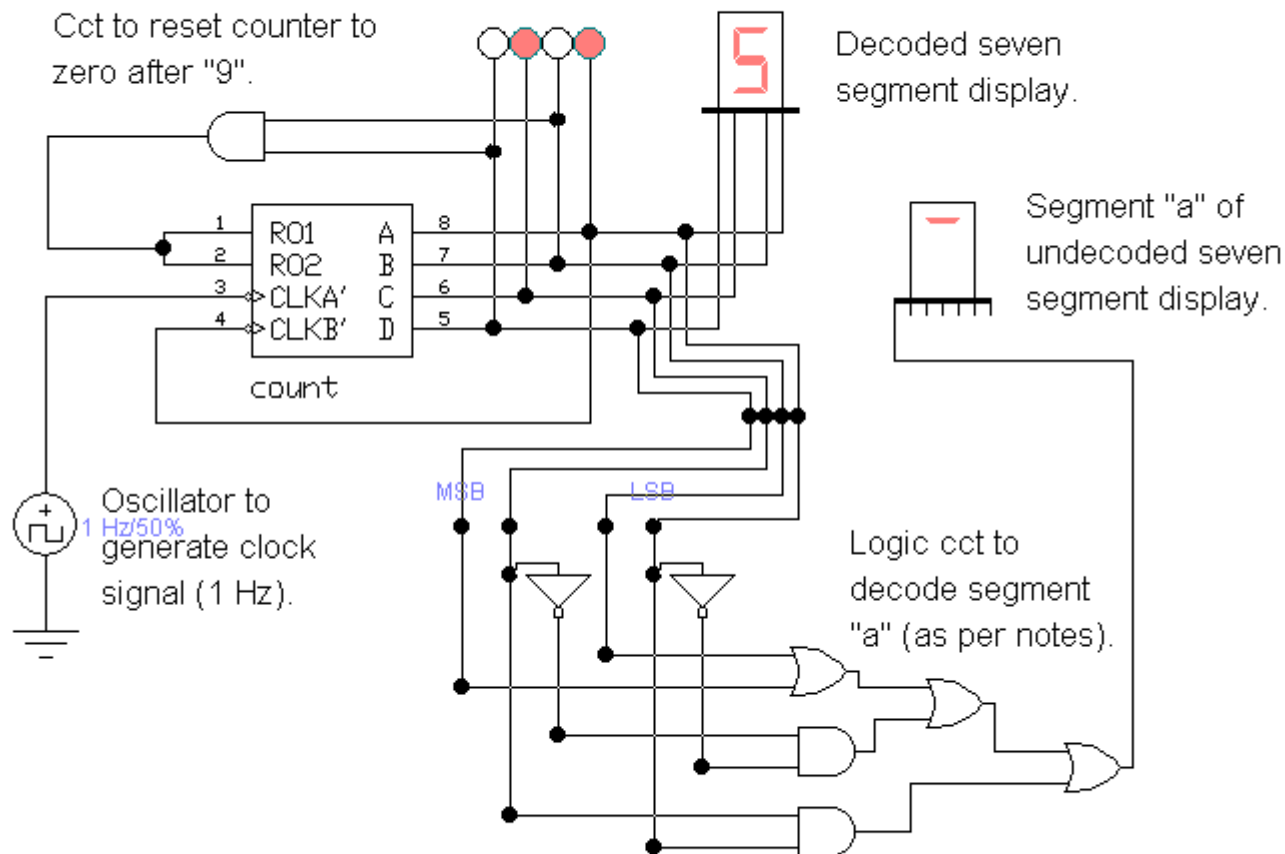Example of seven segment display decoding.



Hint: Select a component and then push "?" from main menu bar to get info on what that component does and how it works.

BCD to seven segment display

- ° Derive the truth table for the circuit.
- ° Each output column in one circuit.

	Inputs				Outputs					
Dec	w	x	y	z	a	b	c	d	e	.
0	0	0	0	0	1	1	1	1	1	.
1	0	0	0	1	0	1	1	0	0	.
2	0	0	1	0	1	1	0	1	1	.
.
7	0	1	1	1	1	1	1	0	0	.
8	1	0	0	0	1	1	1	1	1	.
9	1	0	0	1	1	1	1	1	0	.

BCD to seven segment display

- Find minimal sum-of-products representation for each **output**

For segment “b” :

		yz			
wx		00	01	11	10
	00	1	1	1	1
	01	1	0	1	0
	11				
	10	1	1		

See if you
complete this
example.


Summary

- **Need to formulate circuits from problem descriptions**
 - 1. Determine number of inputs and outputs**
 - 2. Determine truth table format**
 - 3. Determine K-map**
 - 4. Determine minimal SOP**
- **There may be multiple outputs per design**
 - **Solve each output separately**
- **Current approach doesn't have **memory**.**
 - **This will be covered next week.**


Multiplexers

Multiplexers

 - Select an input value with one or more select bits
- Use for transmitting data
- Allows for **conditional** transfer of data
- Sometimes called a **mux**




(a) Logic diagram

 


(b) Block diagram

Fig. 4-24 2-to-1-Line Multiplexer

4- to 1- Line Multiplexer

 

Quadruple 2-to-1-Line Multiplexer

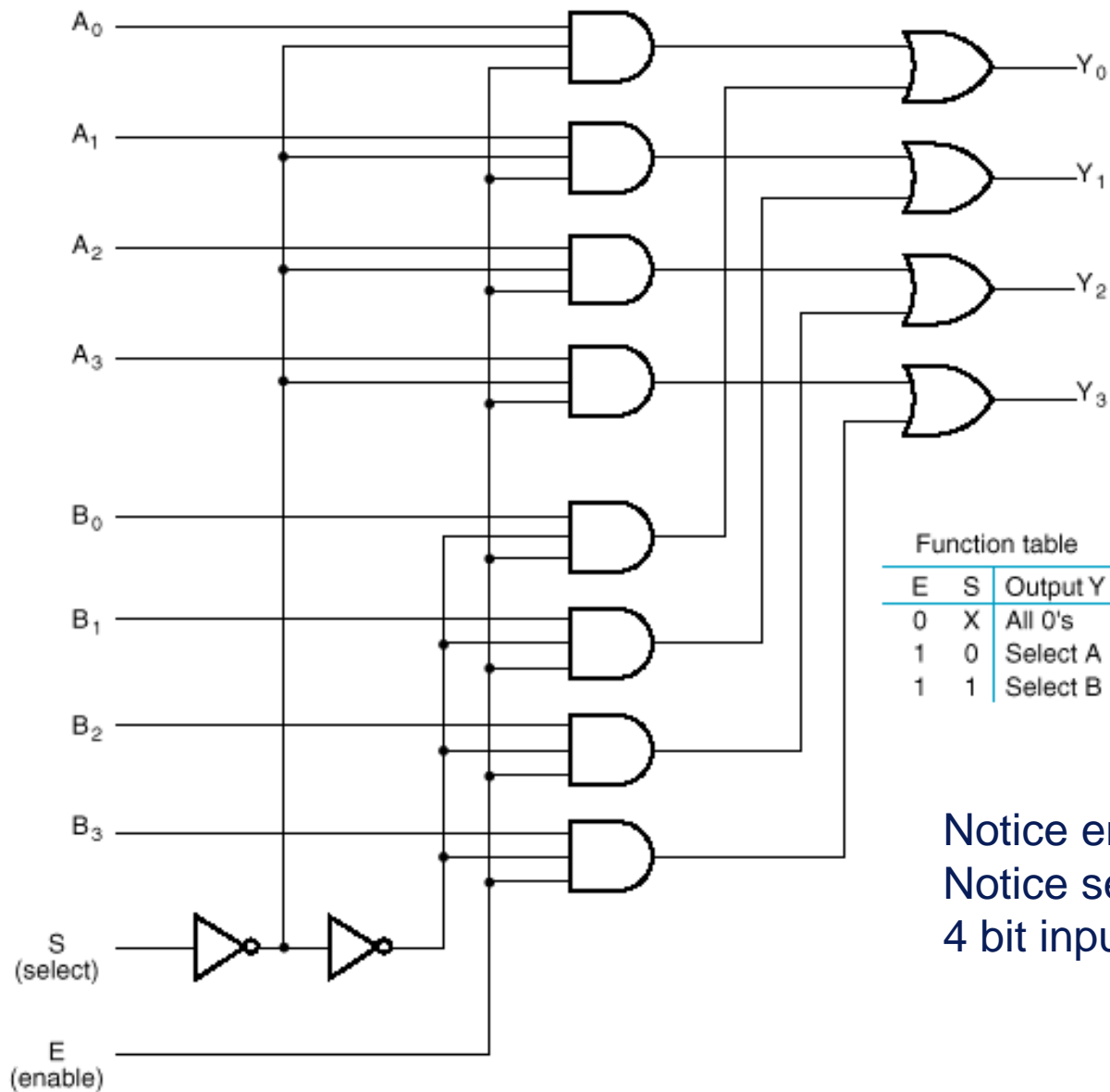


Multiplexer as combinational modules

- Connect input variables to select inputs of multiplexer ($n-1$ for n variables)
- Set data inputs to multiplexer equal to values of function for corresponding assignment of select variables
- Using a variable at data inputs reduces size of the multiplexer

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

(a) Truth table

 


(b) Multiplexer implementation

Fig. 4-27 Implementing a Boolean Function with a Multiplexer

Implementing a Four- Input Function with a Multiplexer

A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = \bar{D}$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

 

Typical multiplexer uses


 


Figure 9.21: Multiplexer example of use.

Three-state gates

 
- A multiplexer can be constructed with three-state gates
- Output state: 0, 1, and high-impedance (open ckts)
- If the select input (E) is 0, the three-state gate has **no output**



Opposite true here,
No output if \bar{E} is 1

\bar{E}	x
0	A
1	Hi-Z

(a)

 


E	x
0	Hi-Z
1	A


(b)

Three-state gates

 - A multiplexer can be constructed with three-state gates
- Output state: 0, 1, and high-impedance



(a) 2-to-1- line mux

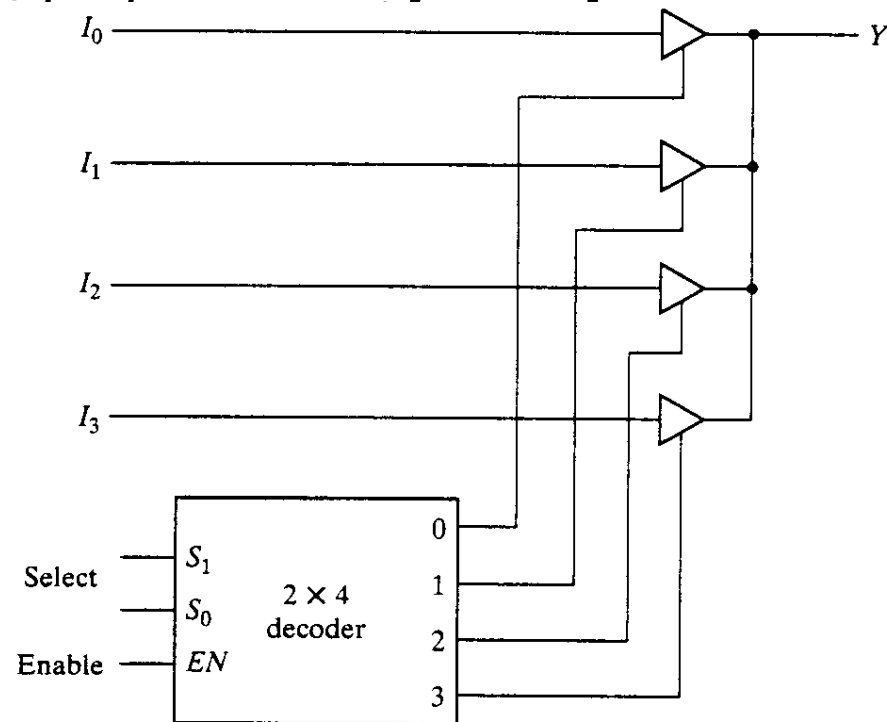

(b) 4 - to - 1 line mux


Encoders and Decoders

Overview

- **Binary decoders**
 - **Converts an n-bit code to a single active output**
 - **Can be developed using AND/OR gates**
 - **Can be used to implement logic circuits.**
- **Binary encoders**
 - **Converts one of 2^n inputs to an n-bit output**
 - **Useful for compressing data**
 - **Can be developed using AND/OR gates**
- **Both encoders and decoders are extensively used in digital systems**

Binary Decoder

 - **Black box with n input lines and 2^n output lines**
- **Only one output is a 1 for any given input**





2-to-4 Binary Decoder

Truth Table:

X	Y	F ₀	F ₁	F ₂	F ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 
 
- From truth table, circuit for 2x4 decoder is:
- Note: Each output is a 2-variable minterm ($X'Y'$, $X'Y$, XY' or XY)



3-to-8 Binary Decoder

Truth Table:

x	y	z	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

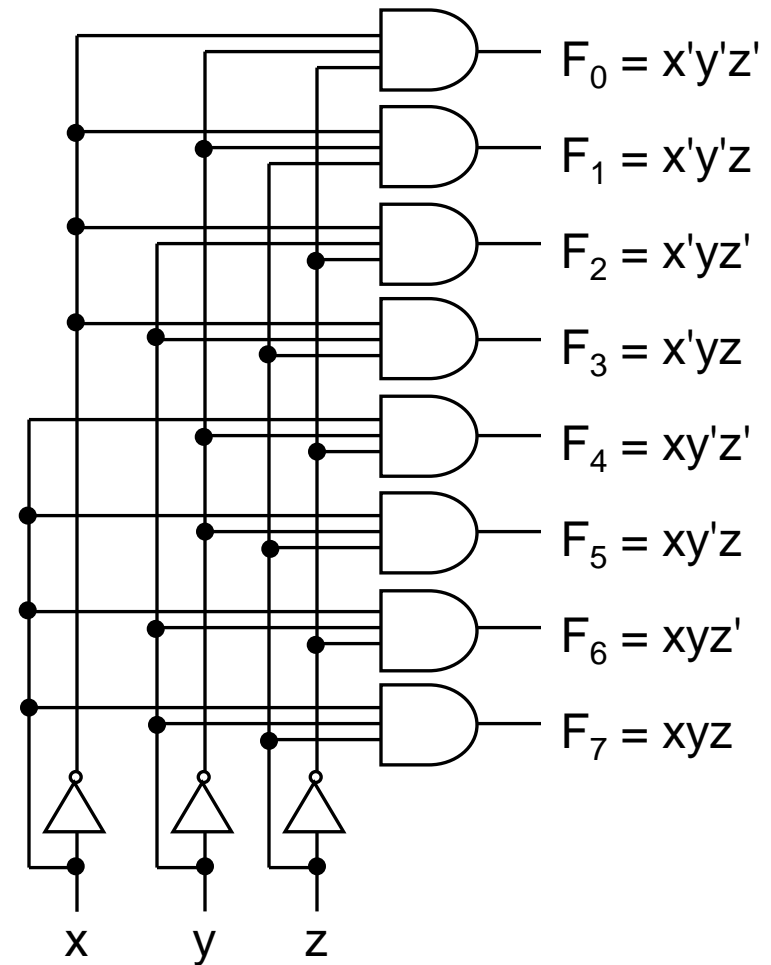 

Implementing Functions Using Decoders

- Any n -variable logic function can be implemented using a single n -to- 2^n decoder to generate the minterms
 - OR gate forms the sum.
 - The output lines of the decoder corresponding to the minterms of the function are used as inputs to the or gate.
- Any combinational circuit with n inputs and m outputs can be implemented with an n -to- 2^n decoder with m OR gates.
- Suitable when a circuit has many outputs, and each output function is expressed with few minterms.


Implementing Functions Using Decoders

° Example: Full adder

$$S(x, y, z) = \Sigma (1,2,4,7)$$


$$C(x, y, z) = \Sigma (3,5,6,7)$$

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


Standard MSI Binary Decoders Example

74138 (3-to-8 decoder)

 

(a)

(a) Logic circuit.

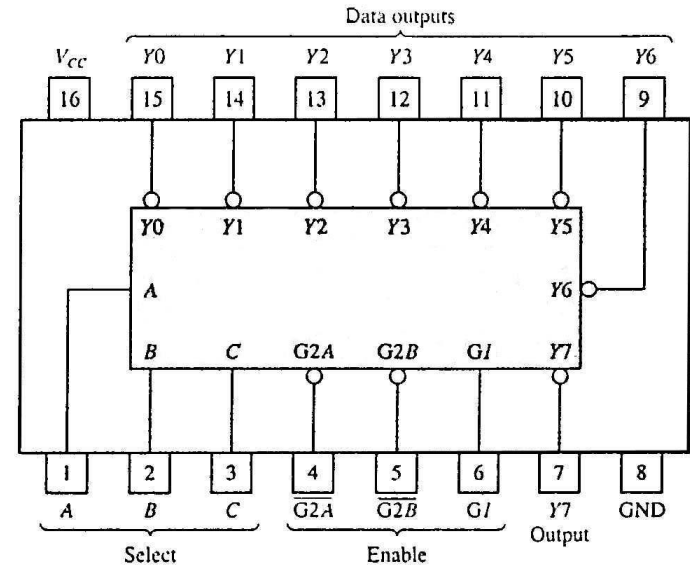

(b)

(b) Package pin configuration.

Inputs			Outputs									
Enable		Select										
G1	$\overline{G2}^*$	C	B	A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
H	L	L	L	L	L	H	H	H	H	H	H	H
H	L	L	L	H	H	L	H	H	H	H	H	H
H	L	L	H	L	H	H	L	H	H	H	H	H
H	L	L	H	H	H	H	L	H	H	H	H	H
H	L	H	L	L	H	H	H	H	L	H	H	H
H	L	H	L	H	H	H	H	H	H	L	H	H
H	L	H	H	L	H	H	H	H	H	H	L	H
H	L	H	H	H	H	H	H	H	H	H	H	L
x	H	x	x	x	H	H	H	H	H	H	H	H
L	x	x	x	x	H	H	H	H	H	H	H	H

$$\overline{G2}^* = \overline{G2A} + \overline{G2B}$$

(c)

(c) Function table.

Building a Binary Decoder with NAND Gates


- **Start with a 2-bit decoder**

- Add an enable signal (E)

Note: use of NANDs

only one 0 active!

if $E = 0$

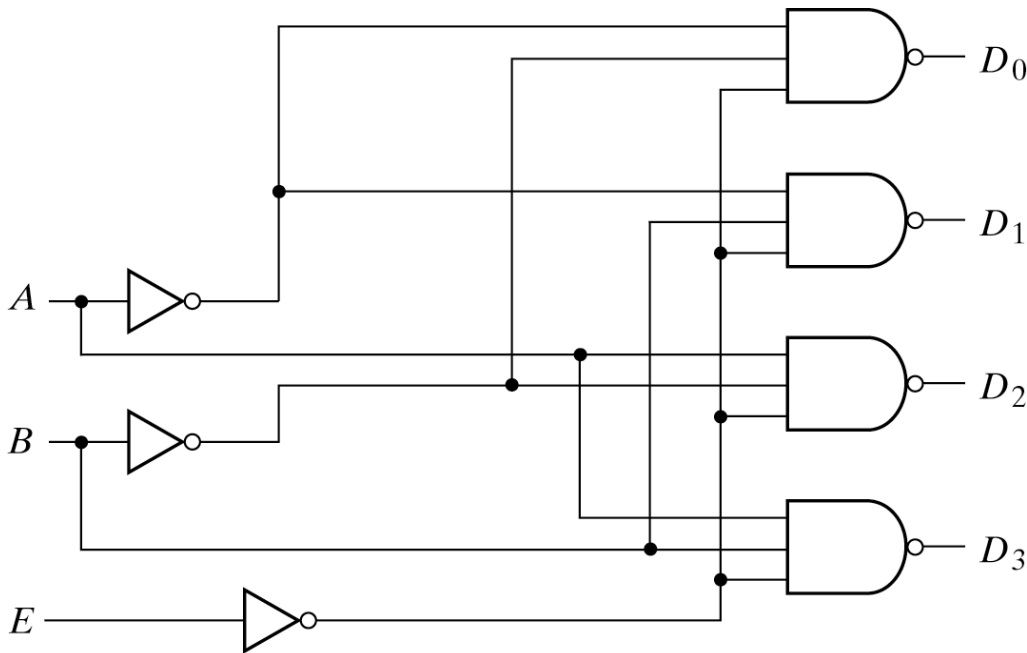

(a) Logic diagram

<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃
1	<i>X</i>	<i>X</i>	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table

Fig. 4-19 2-to-4-Line Decoder with Enable Input

Use two 3 to 8 decoders to make 4 to 16 decoder

- ° Enable can also be active high
- ° In this example, only one decoder can be active at a time.
- ° **x, y, z** effectively select output line for **w**

 



Fig. 4-20 4×16 Decoder Constructed with Two 3×8 Decoders

Encoders

- If the a decoder's output code has fewer bits than the input code, the device is usually called an encoder.

e.g. 2^n -to- n

 
- The simplest encoder is a 2^n -to- n binary encoder
 - One of 2^n inputs = 1
 - Output is an n -bit binary number



8-to-3 Binary Encoder

At any one time, only one input line has a value of 1.

Inputs								Outputs		
I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇	y ₂	y ₁	y ₀
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

 

8-to-3 Priority Encoder

- What if more than one input line has a value of 1?
- Ignore “lower priority” inputs.
- Idle indicates that no input is a 1.
- Note that polarity of Idle is opposite from Table 4-8 in Mano

Inputs								Outputs			
I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇	y ₂	y ₁	y ₀	Idle
0	0	0	0	0	0	0	0	x	x	x	1
1	0	0	0	0	0	0	0	0	0	0	0
X	1	0	0	0	0	0	0	0	0	1	0
X	X	1	0	0	0	0	0	0	1	0	0
X	X	X	1	0	0	0	0	0	1	1	0
X	X	X	X	1	0	0	0	1	0	0	0
X	X	X	X	X	1	0	0	1	0	1	0
X	X	X	X	X	X	1	0	1	1	0	0
X	X	X	X	X	X	X	1	1	1	1	0

Priority Encoder (8 to 3 encoder)

- Assign priorities to the inputs
- When more than one input are asserted, the output generates the code of the input with the highest priority

- Priority Encoder :

$H7=I7$ (Highest Priority)

$H6=I6.I7'$

$H5=I5.I6'.I7'$

$H4=I4.I5'.I6'.I7'$

$H3=I3.I4'.I5'.I6'.I7'$

$H2=I2.I3'.I4'.I5'.I6'.I7'$

$H1=I1.I2'.I3'.I4'.I5'.I6'.I7'$

$H0=I0.I1'.I2'.I3'.I4'.I5'.I6'.I7'$


$IDLE= I0'.I1'.I2'.I3'.I4'.I5'.I6'.I7'$

- Encoder

$Y0 = I1 + I3 + I5 + I7$


$Y1 = I2 + I3 + I6 + I7$

$Y2 = I4 + I5 + I6 + I7$

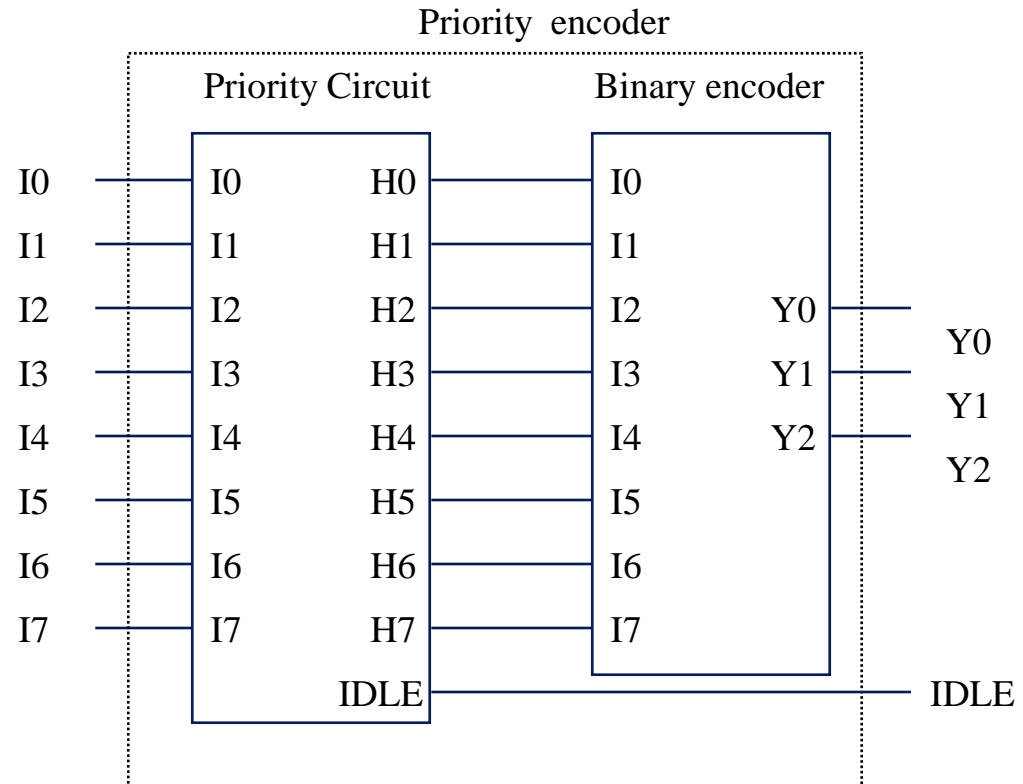

Encoder Application (Monitoring Unit)

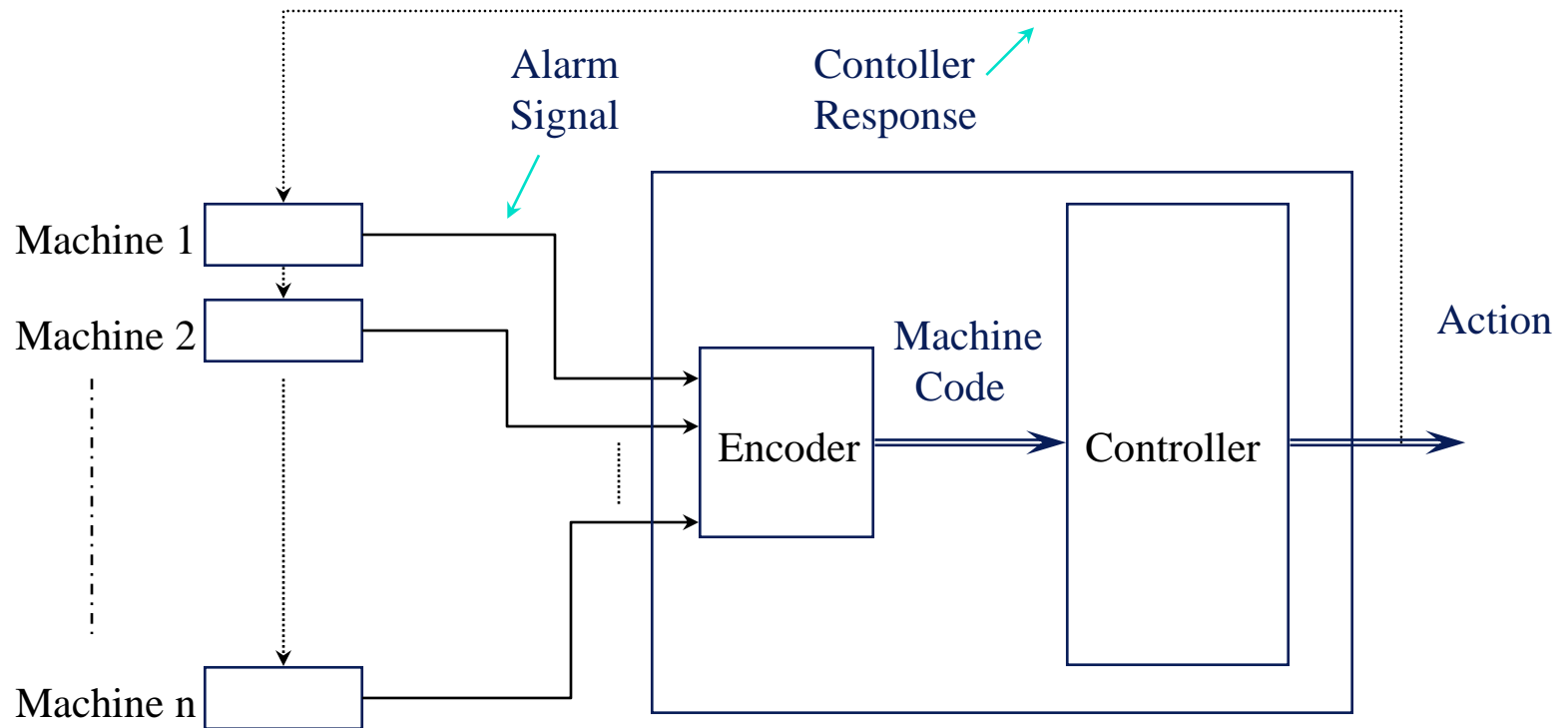Encoder identifies the requester and encodes the value
Controller accepts digital inputs.



Summary

- Decoder allows for generation of a single binary output from an input binary code
 - For an **n**-input binary decoder there are **2^n** outputs
- Decoders are widely used in storage devices (e.g. memories)
 - We will discuss these in a few weeks
- Encoders all for data compression
- Priority encoders rank inputs and encode the highest priority input
- Next time: **storage elements!**