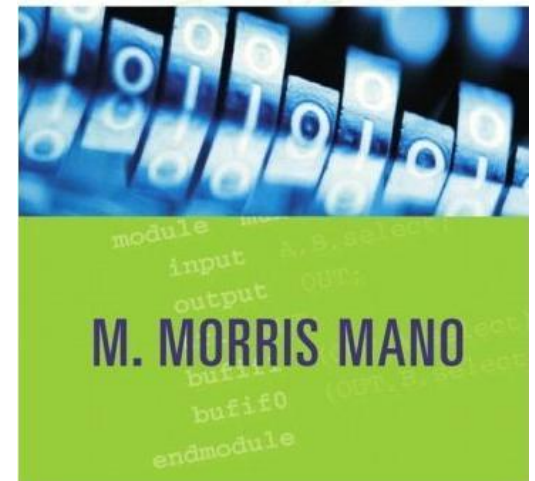


---

**DIGITAL DESIGN**  
THIRD EDITION



**Digital Design 3e, Morris Mano**

**Chapter 3 – Gate Level Minimization**

# COMBINATIONAL CIRCUITS

# Overview

---

- **K-maps: an alternate approach to representing Boolean functions**
- **K-map representation can be used to minimize Boolean functions**
- **Easy conversion from truth table to K-map to minimized SOP representation.**
- **Simple rules (steps) used to perform minimization**
- **Leads to minimized SOP representation.**
  - **Much faster and more more efficient than previous minimization techniques with Boolean algebra.**

# Karnaugh maps

---

- **Alternate way of representing Boolean function**
  - All rows of truth table represented with a square
  - Each square represents a minterm
- **Easy to convert between truth table, K-map, and SOP**
  - Unoptimized form: number of 1's in K-map equals number of minterms (products) in SOP
  - Optimized form: reduced number of minterms

		y	
		0	1
x	0	$x'y'$	$x'y$
	1	$xy'$	$xy$



$$F = \Sigma(m_0, m_1) = x'y + x'y'$$

		y	
		0	1
x	0	1	1
	1	0	0


x	y	F
0	0	1
0	1	1
1	0	0
1	1	0
  
# Karnaugh Maps

- A Karnaugh map is a graphical tool for assisting in the general simplification procedure.
- Two variable maps.



- Three variable maps.

 

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$F = AB'C' + AB'C + ABC + ABC' + A'B'C + A'BC'$$

## Rules for K-Maps

---

- We can reduce functions by **circling** 1's in the K-map
- Each circle represents minterm reduction
- Following circling, we can deduce minimized and-or form.

### Rules to consider

- Every cell containing a 1 must be included at least once.
- The largest possible “power of 2 rectangle” must be enclosed.
- The 1's must be enclosed in the smallest possible number of rectangles.

→  
**Example**

# Karnaugh Maps

---

- ° A Karnaugh map is a graphical tool for assisting in the general simplification procedure.
- ° Two variable maps.

		B	
		0	1
A	0	0	1
	1	1	0

$$F = AB' + A'B$$

		B	
		0	1
A	0	0	1
	1	1	1

$$F = AB + A'B + AB'$$
$$F = A + B$$

- ° Three variable maps.

		BC			
		00	01	11	10
A	0	0	1	0	1
	1	1	1	1	1

$$F = A + B'C + BC'$$

$$F = AB'C' + AB'C + ABC + ABC' + A'B'C + A'BC'$$

# Karnaugh maps

## ◦ Numbering scheme based on Gray-code

- e.g., 00, 01, 11, 10
- Only a single bit changes in code for adjacent map cells
- This is necessary to observe the variable transitions

		A	
		1	1
C	0	0	1
	0	0	1
		B	

$$G(A,B,C) = A$$





		AB		A	
		00	01	11	10
C	0				
	1				
		B			

		A	
		1	1
C	0	0	1
	0	0	1
		B	

$$F(A,B,C) = \sum m(0,4,5,7) = AC + B'C'$$

# More Karnaugh Map Examples


## ◦ Examples

    

1. Circle the largest groups possible.
2. Group dimensions must be a power of 2.
3. Remember what circling means!


 
# Application of Karnaugh Maps: The One-bit Adder



A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

How to use a Karnaugh Map instead of the Algebraic simplification?

$$S = A'B'Cin + A'BCin' + A'BCin + ABCin$$

$$Cout = A'BCin + A B'Cin + ABCin' + ABCin$$


$$= A'BCin + ABCin + AB'Cin + ABCin + ABCin' + ABCin$$

$$= (A' + A)BCin + (B' + B)ACin + (Cin' + Cin)AB$$

$$= 1 \cdot BCin + 1 \cdot ACin + 1 \cdot AB$$

$$= BCin + ACin + AB$$
 
# Application of Karnaugh Maps: The One-bit Adder




A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

		A			
		0	0	1	0
B		0	1	1	1
		Cin			

Karnaugh Map for Cout

Now we have to cover all the 1s in the Karnaugh Map using the largest rectangles and as few rectangles as we can.
 
# Application of Karnaugh Maps: The One-bit Adder



A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


				A
				┌───┐
				1
				1
				└───┘
B	┌──┐	┌──┐	┌──┐	┌──┐
└──┘	0	1	1	1
	0	0	1	0
	└──┘	└──┘	└──┘	└──┘
				Cin

Karnaugh Map for Cout


Now we have to cover all the 1s in the Karnaugh Map using the largest rectangles and as few rectangles as we can.

$$\text{Cout} = \text{ACin}$$
 
# Application of Karnaugh Maps: The One-bit Adder



A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


Karnaugh Map for Cout


Now we have to cover all the 1s in the Karnaugh Map using the largest rectangles and as few rectangles as we can.

$$\text{Cout} = \text{Acin} + \text{AB}$$
 
# Application of Karnaugh Maps: The One-bit Adder



A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


Karnaugh Map for Cout


Now we have to cover all the 1s in the Karnaugh Map using the largest rectangles and as few rectangles as we can.

$$\text{Cout} = \text{ACin} + \text{AB} + \text{BCin}$$
 
# Application of Karnaugh Maps: The One-bit Adder




A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


$$S = A'BC_{in}'$$

Karnaugh Map for  $S$
 
# Application of Karnaugh Maps: The One-bit Adder




$A$	$B$	$C_{in}$	$S$	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


Karnaugh Map for  $S$

$$S = A'BC_{in}' + A'B'C_{in}$$
 
# Application of Karnaugh Maps: The One-bit Adder



$A$	$B$	$C_{in}$	$S$	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


$$S = A'B'C_{in}' + A'B'C_{in} + \textcolor{red}{A}B\textcolor{red}{C}_{in}$$

Karnaugh Map for  $S$




# Application of Karnaugh Maps: The One-bit Adder

Can you draw the circuit diagrams?

 

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

Karnaugh Map for S

$$S = A'BCin' + A'B'Cin + ABCin + AB'Cin'$$

No Possible Reduction!

# Summary

---

- Karnaugh map allows us to represent functions with new notation
- Representation allows for logic reduction.
  - Implement same function with less logic
- Each square represents one minterm
- Each circle leads to one product term
- Not all functions can be reduced
- Each circle represents an application of:
  - Distributive rule --  $x(y + z) = xy + xz$
  - Complement rule –  $x + x' = 1$

---

***More Karnaugh Maps and Don't Cares***

# Overview

---

- **Karnaugh maps with four inputs**
  - Same basic rules as three input K-maps
- **Understanding prime implicants**
  - Related to minterms
- **Covering all implicants**
- **Using Don't Cares to simplify functions**
  - Don't care outputs are undefined
- **Summarizing Karnaugh maps**

# Karnaugh Maps for Four Input Functions

- Represent functions of 4 inputs with 16 minterms
- Use same rules developed for 3-input functions
- Note bracketed sections shown in example.

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$
$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
$m_8$	$m_9$	$m_{11}$	$m_{10}$

(a)

		$yz$		$y$	
		00	01	11	10
$wx$	00	$w'x'y'z'$	$w'x'y'z$	$w'x'yz$	$w'x'yz'$
	01	$w'xy'z'$	$w'xy'z$	$w'xyz$	$w'xyz'$
	11	$wxy'z'$	$wxy'z$	$wxyz$	$wxyz'$
	10	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$
		$z$			

(b)

Fig. 3-8 Four-variable Map


# Karnaugh map: 4-variable example

°  $F(A,B,C,D) = \sum m(0,2,3,5,6,7,8,10,11,14,15)$

$F =$

$$C + A'BD + B'D'$$

				A	
C	1	0	0	1	D
	0	1	0	0	
	1	1	1	1	
	1	1	1	1	
				B	

 

Solution set can be considered as a coordinate System!

# Design examples

---

	A				
	0	0	0	0	
	1	0	0	0	D
	1	1	0	1	
C	1	1	0	0	
	1	1	0	0	
	B				

K-map for LT

	A				
	1	0	0	0	
	0	1	0	0	D
	0	0	1	0	
C	0	0	0	1	
	0	0	0	1	
	B				

K-map for EQ

	A				
	0	1	1	1	
	0	0	1	1	D
	0	0	0	0	
C	0	0	1	0	
	0	0	1	0	
	B				

K-map for GT


$$LT = A' B' D + A' C + B' C D$$

$$EQ = A' B' C' D' + A' B C' D + A B C D + A B' C D'$$

$$GT = B C' D' + A C' + A B D'$$

Can you draw the truth table for these examples?

# Physical Implementation

 

- Step 1: Truth table
- Step 2: K-map
- Step 3: Minimized sum-of-products
- Step 4: Physical implementation with gates

A				D
1	0	0	0	
0	1	0	0	
0	0	1	0	
C	0	0	0	1
	0	0	0	1
B				

K-map for EQ



# Karnaugh Maps

---

- Four variable maps.

		CD			
		00	01	11	10
AB	00	0	0	0	1
	01	1	1	0	1
	11	1	1	1	1
	10	1	0	1	1

$$F = A'BC' + A'CD' + ABC \\ + AB'C'D' + ABC' + AB'C$$

$$F = BC' + CD' + AC + AD'$$

- Need to make sure all 1's are covered
- Try to minimize total product terms.
- Design could be implemented using NANDs and NORs

## Karnaugh maps: Don't cares

---

- In some cases, outputs are undefined
- We “don't care” if the logic produces a 0 or a 1
- This knowledge can be used to simplify functions.

		A			
		00	01	11	10
C	00	0	0	X	0
	01	1	1	X	1
	11	1	1	0	0
	10	0	X	0	0

- Treat X's like either 1's or 0's
- Very useful
- OK to leave some X's uncovered

# Karnaugh maps: Don't cares

◦  $f(A,B,C,D) = \sum m(1,3,5,7,9) + d(6,12,13)$

- without don't cares

-  $f =$

$A'D + C'D$

		<u>A</u>			
		AB			
		00	01	11	10
CD	00	0	0	X	0
	01	1	1	X	1
	11	1	1	0	0
	10	0	X	0	0
		<u>B</u>			
		D			
		C			

A	B	C	D	f
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	X
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	X
1	1	0	1	X
1	1	1	0	0
1	1	1	1	0

# Karnaugh maps: don't cares (cont'd)

◦  $f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$

•  $f = A'D + B'C'D$

without don't cares

•  $f =$

with don't cares

$A'D + C'D$

				A	
		0	0	X	0
		1	1	X	1
		1	1	0	0
		0	X	0	0
C					D
				B	

by using don't care as a "1"  
a 2-cube can be formed  
rather than a 1-cube to cover  
this node

don't cares can be treated as  
1s or 0s

depending on which is more  
advantageous

# Don't Care Conditions

---

- In some situations, we don't care about the value of a function for certain combinations of the variables.
  - these combinations may be impossible in certain contexts
  - or the value of the function may not matter in when the combinations occur
- In such situations we say the function is *incompletely specified* and there are multiple (completely specified) logic functions that can be used in the design.
  - so we can select a function that gives the simplest circuit
- When constructing the terms in the simplification procedure, we can choose to either cover or not cover the don't care conditions.

# Map Simplification with Don't Cares

$AB \backslash CD$		$CD$			
		00	01	11	10
00	00	0	1	0	0
01	01	x	x	x	1
11	11	1	1	1	x
10	10	x	0	1	1

$F=A'C'D+B+AC$

◦ **Alternative covering.**

$AB \backslash CD$		$CD$			
		00	01	11	10
00	00	0	1	0	0
01	01	x	x	x	1
11	11	1	1	1	x
10	10	x	0	1	1

$F=A'B'C'D+ABC'+BC+AC$

# Definition of terms for two-level simplification

---

## ◦ Implicant

- Single product term of the **ON-set** (terms that create a logic 1)

## ◦ Prime implicant

- Implicant that can't be combined with another to form an implicant with fewer literals.

## ◦ Essential prime implicant

- Prime implicant is essential if it alone covers a minterm in the K-map
- Remember that all squares marked with 1 must be covered

## ◦ Objective:

- Grow implicant into prime implicants (minimize literals per term)
- Cover the K-map with as few prime implicants as possible (minimize number of product terms)

# Examples to illustrate terms

				A
	0	X	1	0
	1	1	1	0
C	1	0	1	1
	0	0	1	1
				B

6 prime implicants:

$A'B'D$ ,  $BC'$ ,  $AC$ ,  $A'C'D$ ,  $AB$ ,  $B'CD$

essential

minimum cover:  $AC + BC' + A'B'D$

5 prime implicants:

$BD$ ,  $ABC'$ ,  $ACD$ ,  $A'BC$ ,  $A'C'D$

essential

minimum cover: 4 essential implicants

				A
	0	0	1	0
	1	1	1	0
	0	1	1	1
C	0	1	0	0
				B




# Prime Implicants

Any single 1 or group of 1s in the Karnaugh map of a function  $F$  is an implicant of  $F$ .

A product term is called a prime implicant of  $F$  if it cannot be combined with another term to eliminate a variable.

Example:

 

If a function  $F$  is represented by this Karnaugh Map. Which of the following terms are implicants of  $F$ , and which ones are prime implicants of  $F$ ?

- (a)  $AC'D'$
- (b)  $BD$
- (c)  $A'B'C'D'$
- (d)  $AC'$
- (e)  $B'C'D'$


Implicants:  
(a),(c),(d),(e)

Prime Implicants:  
(d),(e)

 
# Essential Prime Implicants

A product term is an essential prime implicant if there is a minterm that is only covered by that prime implicant.

- The minimal sum-of-products form of  $F$  must include all the essential prime implicants of  $F$ .



 (a) Essential prime implicants  
 $BD$  and  $B'D'$



(b) Prime implicants  $CD$ ,  $B'C$ ,  
 $AD$ , and  $AB'$

Fig. 3-11 Simplification Using Prime Implicants

## Solution

---

$$\begin{aligned} F &= BD + B'D' + CD + AD \\ &= BD + B'D' + CD + AB' \\ &= BD + B'D' + B'C + AD \\ &= BD + B'D' + B'C + AB' \end{aligned}$$

# Summary

---

- **K-maps of four literals considered**
  - **Larger examples exist**
- **Don't care conditions help minimize functions**
  - **Output for don't cares are undefined**
- **Result of minimization is minimal sum-of-products**
- **Result contains prime implicants**
- **Essential prime implicants are required in the implementation**

---

## ***NAND and XOR Implementations***

# Overview

---

- **Developing NAND circuits from K-maps**
- **Two-level implementations**
  - Convert from AND/OR to NAND (again!)
- **Multi-level NAND implementations**
  - Convert from a network of AND/ORs
- **Exclusive OR**
  - Comparison with SOP
- **Parity checking and detecting circuitry**
  - Efficient with XOR gates!


# NAND-NAND & NOR-NOR Networks

---
 
## DeMorgan's Law:

$$(a + b)' = a' b' \quad (a b)' = a' + b'$$

$$a + b = (a' b')' \quad (a b) = (a' + b')'$$







***push bubbles or introduce in pairs or remove pairs.***

# NAND-NAND Networks

---

## ° Mapping from AND/OR to NAND/NAND

    




# Implementations of Two-level Logic

---

 
## ◦ Sum-of-products

- AND gates to form product terms (minterms)
- OR gate to form sum


 
## ◦ Product-of-sums



- OR gates to form sum terms (maxterms)
- AND gates to form product


  
## Two-level Logic using NAND Gates

---

- Replace minterm AND gates with NAND gates
- Place compensating inversion at inputs of OR gate



## Two-level Logic using NAND Gates (cont'd)




---

- **OR gate with inverted inputs is a NAND gate**

- de Morgan's:  $A' + B' = (A \cdot B)'$

- **Two-level NAND-NAND network**

  
 
- Inverted inputs are not counted
- In a typical circuit, inversion is done once and signal distributed


  
# Conversion Between Forms



---

- **Convert from networks of ANDs and ORs to networks of NANDs and NORs**
  - Introduce appropriate inversions ("bubbles")
- **Each introduced "bubble" must be matched by a corresponding "bubble"**
  - Conservation of inversions
  - Do not alter logic function
- **Example: AND/OR to NAND/NAND**



## Conversion Between Forms (cont'd)

  
- **Example: verify equivalence of two forms**




$$\begin{aligned} Z &= [ (A \cdot B)' \cdot (C \cdot D)' ]' \\ &= [ (A' + B') \cdot (C' + D') ]' \\ &= [ (A' + B')' + (C' + D')' ] \\ &= (A \cdot B) + (C \cdot D) \checkmark \end{aligned}$$
 
# Conversion to NAND Gates


- **Start with SOP (Sum of Products)**
  - circle 1s in K-maps
- **Find network of OR and AND gates**



(a) AND\_OR network

 

(b) First step in NAND conversion

 


(c) Completed conversion
 
# Multi-level Logic


---

- $x = A D F + A E F + B D F + B E F + C D F + C E F + G$ 
  - Reduced sum-of-products form – already simplified
  - 6 x 3-input AND gates + 1 x 7-input OR gate (may not exist!)
  - 25 wires (19 literals plus 6 internal wires)
- $x = (A + B + C) (D + E) F + G$ 
  - Factored form – not written as two-level S-o-P
  - 1 x 3-input OR gate, 2 x 2-input OR gates, 1 x 3-input AND gate
  - 10 wires (7 literals plus 3 internal wires)



# Conversion of Multi-level Logic to NAND Gates





°  $F = A(B + CD) + BC'$

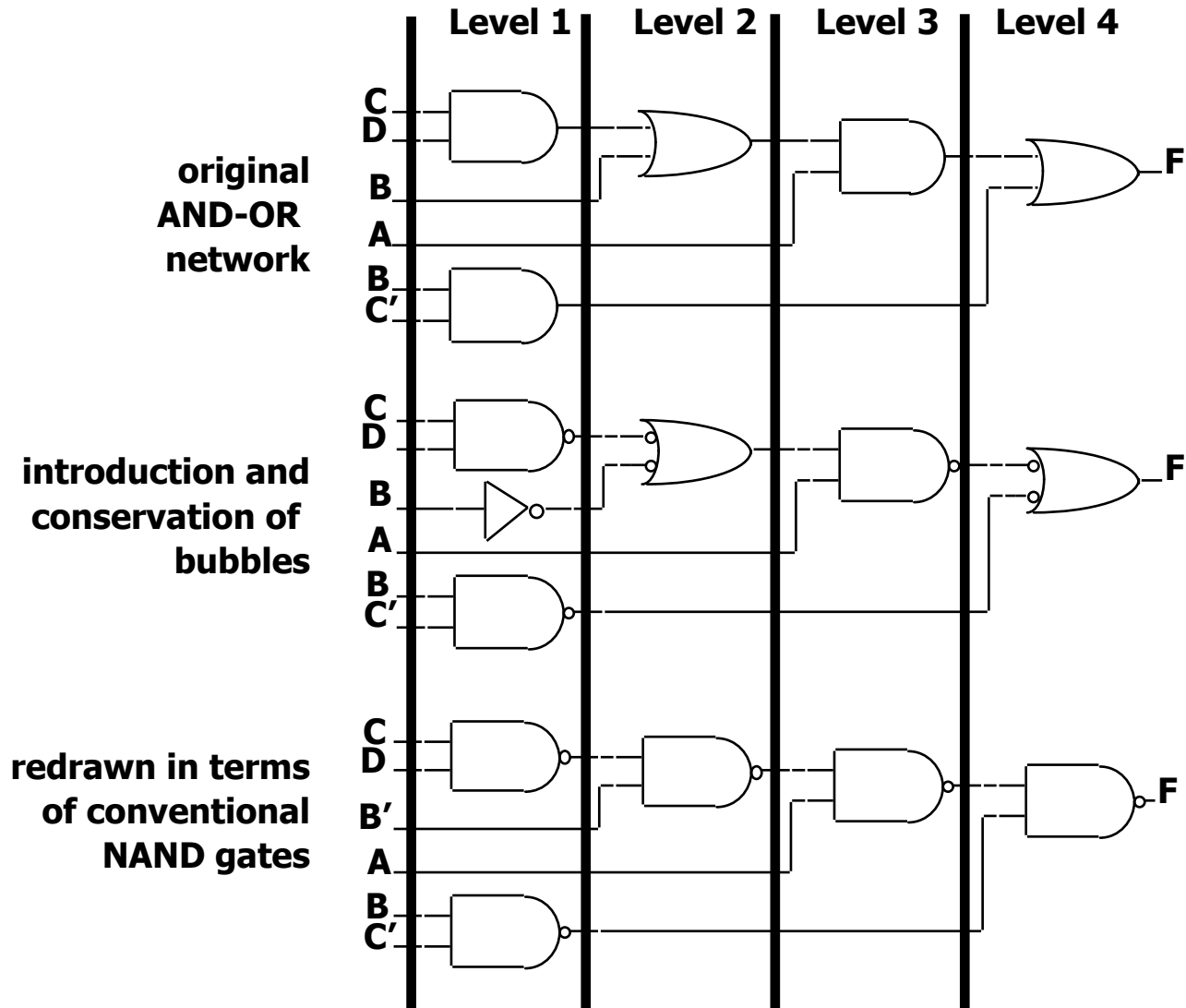




# Conversion Between Forms

## ◦ Example

   
 

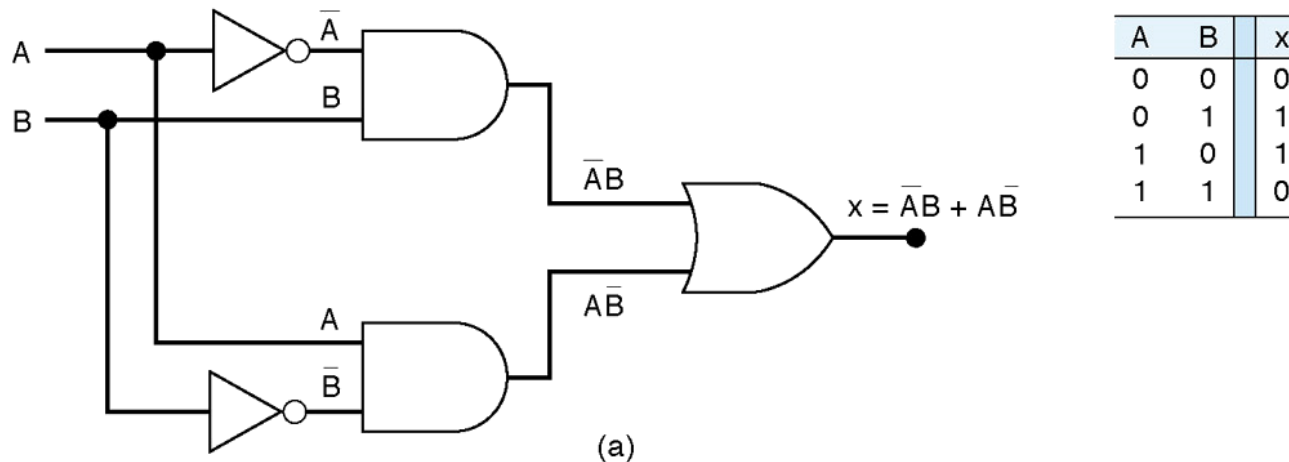
# Exclusive-OR and Exclusive-NOR Circuits

Exclusive-OR (XOR) produces a HIGH output whenever the two inputs are at opposite levels.




XOR gate symbols

  

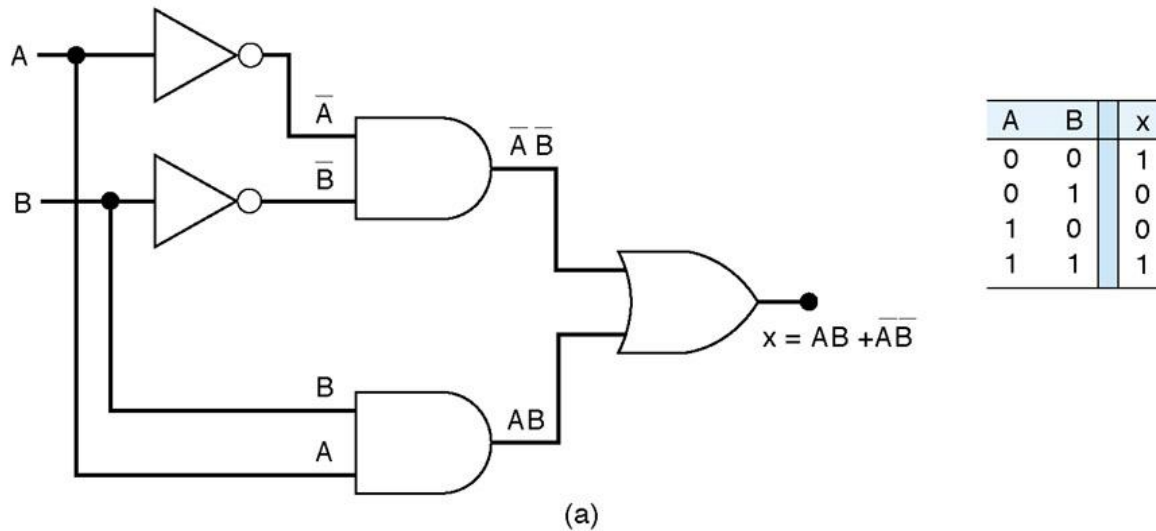
# Exclusive-NOR Circuits

Exclusive-NOR (XNOR) :


Exclusive-NOR (XNOR) produces a HIGH output whenever the two inputs are at the same level.



XNOR gate symbols

 


(b)

 


(c)
 
# Exclusive-NOR Circuits

XNOR gate may be used to simplify circuit implementation.




(a)

 


(b)
 
# XOR Function

- ° XOR function can also be implemented with AND/OR gates (also NANDs).



(a) With AND-OR-NOT gates

 

(b) With NAND gates

Fig. 3-32 Exclusive-OR Implementations

- 
- ° The first NAND gate performs the operation

$$(xy)' = (x' + y').$$

- ° The other two-level NAND circuit produces the **sum** of products of its inputs:

$$(x' + y')x + (x' + y')y = xy' + x'y = x \text{ XOR } y$$

# XOR Function

- Even function – even number of inputs are 1.
- Odd function – odd number of inputs are 1.

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0		1		1
	1	1		1	

(a) Odd function  
 $F = A \oplus B \oplus C$


		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1		1	
	1		1		1

(a) Even function  
 $F = (A \oplus B \oplus C)'$

Fig. 3-33 Map for a Three-variable Exclusive-OR Function

# Parity Generation and Checking

**FIGURE 4-25** XOR gates used to implement the parity generator and the parity checker for an even-parity system.

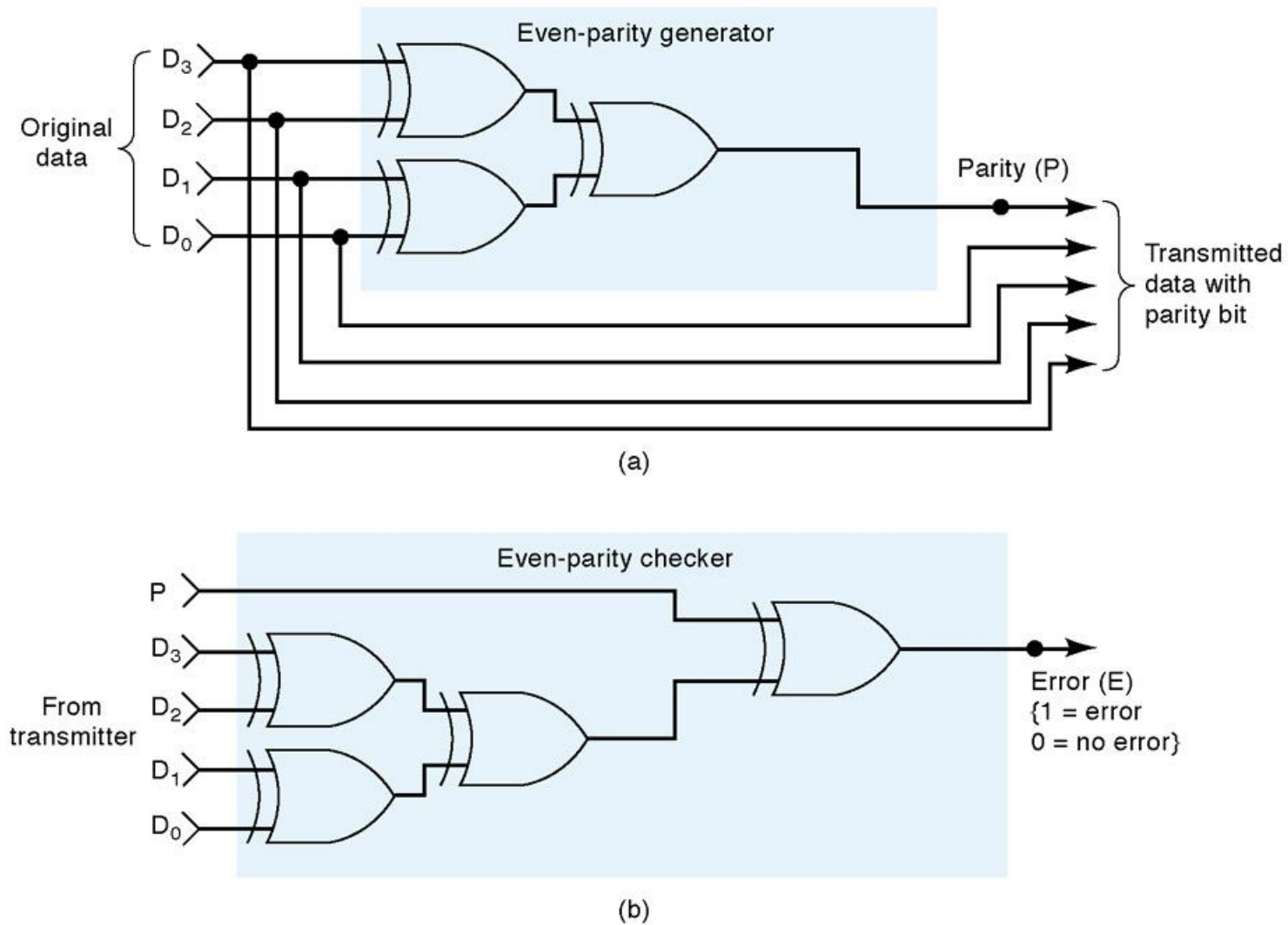




# Summary

---

- Follow rules to convert between AND/OR representation and symbols
- Conversions are based on DeMorgan's Law
- NOR gate implementations are also possible
- XORs provide straightforward implementation for some functions
- Used for parity generation and checking
  - XOR circuits could also be implemented using AND/Ors
- Next time: Hazards

---

**DIGITAL DESIGN**  
THIRD EDITION

 

**Digital Design 3e, Morris Mano**

**Chapter 4 – Combinational Logic**

# **MODULAR DESIGN OF COMBINATIONAL CIRCUITS**

---

## ***Circuit Analysis Procedure***

# Overview


---

- **Important concept – analyze digital circuits**
  - **Given a circuit**
    - **Create a truth table**
    - **Create a minimized circuit**
- **Approaches**
  - **Boolean expression approach**
  - **Truth table approach**
- **Leads to minimized hardware**
- **Provides insights on how to design hardware**
  - **Tie in with K-maps (next time)**
 
# The Problem

---


- How can we convert from a circuit drawing to an equation or truth table?
- Two approaches
  - Create intermediate equations
  - Create intermediate truth tables



# Label Gate Outputs

---

 
1. Label all gate outputs that are a function of input variables.
2. Label gates that are a function of input variables and previously labeled gates.
3. Repeat process until all outputs are labelled.


 
# Approach 1: Create Intermediate Equations

---


- ❑ Step 1: Create an equation for each gate output based on its input.
- $R = ABC$
  - $S = A + B$
  - $T = C'S$
  - $Out = R + T$


 
# Approach 1: Substitute in subexpressions

---

- ❑ Step 2: Form a relationship based on input variables (A, B, C)
  - $R = ABC$
  - $S = A + B$
  - $T = C'S = C'(A + B)$
  - $\text{Out} = R + T = ABC + C'(A + B)$





 
# Approach 1: Substitute in subexpressions

---


- ❑ Step 3: Expand equation to SOP final result
  - **Out =  $ABC + C'(A+B) = ABC + AC' + BC'$**



# Approach 2: Truth Table

- Step 1: Determine outputs for functions of input variables.

A	B	C	R	S
0	0	0	0	0
0	0	1	0	0
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


# Approach 2: Truth Table

- Step 2: Determine outputs for functions of intermediate variables.

$$T = S * C'$$

A	B	C	C'	R	S	T
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	1	1
0	1	1	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	0	1	0
1	1	0	1	0	1	1
1	1	1	0	1	1	0

 


## Approach 2: Truth Table

- Step 3: Determine outputs for function.

$$R + T = \text{Out}$$

A	B	C	R	S	T	Out
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	1	1	1
0	1	1	0	1	0	0
1	0	0	0	1	1	1
1	0	1	0	1	0	0
1	1	0	0	1	1	1
1	1	1	1	1	0	1

 

# More Difficult Example

## □ Step 3: Note labels on interior nodes

 


Fig. 4-2 Logic Diagram for Analysis Example

# More Difficult Example: Truth Table

---

- ❑ Remember to determine intermediate variables starting from the inputs.
- ❑ When all inputs determined for a gate, determine output.
- ❑ The truth table can be reduced using K-maps.

A	B	C	$F_2$	$F'_2$	$T_1$	$T_2$	$T_3$	$F_1$
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

# Summary

---

- Important to be able to convert circuits into truth table and equation form
  - **WHY? ---- leads to minimized sum of product representation**
- Two approaches illustrated
  - **Approach 1: Create an equation with circuit output dependent on circuit inputs**
  - **Approach 2: Create a truth table which shows relationship between circuit inputs and circuit outputs**
- Both results can then be minimized using K-maps.
- Next time: develop a minimized SOP representation from a high level description

---

# ***Combinational Design Procedure***



# Overview

---

- Design digital circuit from specification
- Digital inputs and outputs known
  - Need to determine logic that can *transform* data
- Start in truth table form
- Create K-map for each output based on function of inputs
- Determine minimized sum-of-product representation
- Draw circuit diagram

# Design Procedure (Mano)

---

## Design a circuit from a specification.

1. Determine number of required inputs and outputs.
2. Derive truth table
3. Obtain simplified Boolean functions
4. Draw logic diagram and verify correctness

$$S = A + B + C$$
$$R = ABC$$

A	B	C	R	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## **Previously, we have learned...**

---

- **Boolean algebra can be used to simplify expressions, but not obvious:**
  - **how to proceed at each step, or**
  - **if solution reached is minimal.**
- **Have seen five ways to represent a function:**
  - **Boolean expression**
  - **truth table**
  - **logic circuit**
  - **minterms/maxterms**
  - **Karnaugh map**

# **Combinational logic design**

---


- **Use multiple representations of logic functions**
- **Use graphical representation to assist in simplification of function.**
- **Use concept of “don’t care” conditions.**
- **Example - encoding BCD to seven segment display.**
- **Similar to approach used by designers in the field.**

## BCD to Seven Segment Display

---

- Used to display binary coded decimal (BCD) numbers using seven illuminated segments.
- BCD uses 0's and 1's to represent decimal digits 0 - 9. Need four bits to represent required 10 digits.
- Binary coded decimal (BCD) represents each decimal digit with four bits

0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
.	.	.	.	.
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

 


## BCD to seven segment display

---

- ° List the segments that should be illuminated for each digit.

0	a,b,c,d,e,f
1	b,c
2	a,b,d,e,g
3	a,b,c,d,g
4	b,c,f,g
5	a,c,d,f,g
6	a,c,d,e,f,g
7	a,b,c
8	a,b,c,d,e,f,g
9	a,b,c,d,f,g

 

## BCD to seven segment display

---

- ° Derive the truth table for the circuit.
- ° Each output column in one circuit.

	Inputs				Outputs					
Dec	w	x	y	z	a	b	c	d	e	.
0	0	0	0	0	1	1	1	1	1	.
1	0	0	0	1	0	1	1	0	0	.
2	0	0	1	0	1	1	0	1	1	.
.	.	.	.	.	.	.	.	.	.	.
7	0	1	1	1	1	1	1	0	0	.
8	1	0	0	0	1	1	1	1	1	.
9	1	0	0	1	1	1	1	1	0	.

## BCD to seven segment display

---

- Find minimal sum-of-products representation for each **output**

For segment “a” :

		yz			
wx		00	01	11	10
	00	1	0	1	1
	01	0	1	1	1
	11				
	10	1	1		

Note: Have only filled in ten squares, corresponding to the ten numerical digits we wish to represent.



## Don't care conditions (BCD display) ...

---

- Fill in don't cares for **undefined** outputs.
    - Note that these combinations of inputs should never happen.
  - Leads to a reduced implementation
- For segment "a" :

		yz			
		00	01	11	10
wx	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X

Put in “X” (don't care), and interpret as either 1 or 0 as desired ....

## Don't care conditions (BCD display) ...

---

- Circle biggest group of 1's and Don't Cares.
- Leads to a reduced implementation

For segment “a” :

		yz			
		00	01	11	10
wx	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X

$$F_{a1} = y$$

## Don't care conditions (BCD display)

---

- Circle biggest group of 1's and Don't Cares.
- Leads to a reduced implementation

For segment “a” :

wx \ yz	yz			
	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	X	X	X	X
10	1	1	X	X

$$F_{a2} = w$$

## Don't care conditions (BCD display) ...

- Circle biggest group of 1's and Don't Cares.
- All 1's should be covered by at least one implicant

For segment “a” :

		yz			
		00	01	11	10
wx	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X

$$F_{a3} = \overline{x} \overline{z}$$

		yz			
		00	01	11	10
wx	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X

$$F_{a4} = xz$$

## Don't care conditions (BCD display) ...

---


- Put all the terms together
- Generate the circuit

For segment “a” :

		yz			
		00	01	11	10
wx	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X

$$F = y + w + \overline{\overline{x}}\overline{\overline{z}} + xz$$
 
## Example of seven segment display decoding.



Hint: Select a component and then push "?" from main menu bar to get info on what that component does and how it works.

## BCD to seven segment display

---

- ° Derive the truth table for the circuit.
- ° Each output column in one circuit.

	Inputs				Outputs					
Dec	w	x	y	z	a	b	c	d	e	.
0	0	0	0	0	1	1	1	1	1	.
1	0	0	0	1	0	1	1	0	0	.
2	0	0	1	0	1	1	0	1	1	.
.	.	.	.	.	.	.	.	.	.	.
7	0	1	1	1	1	1	1	0	0	.
8	1	0	0	0	1	1	1	1	1	.
9	1	0	0	1	1	1	1	1	0	.

## BCD to seven segment display

---

- Find minimal sum-of-products representation for each **output**

For segment “b” :

		yz			
wx		00	01	11	10
	00	1	1	1	1
	01	1	0	1	0
	11				
	10	1	1		

See if you  
complete this  
example.



# Summary

---

- **Need to formulate circuits from problem descriptions**
  - 1. Determine number of inputs and outputs**
  - 2. Determine truth table format**
  - 3. Determine K-map**
  - 4. Determine minimal SOP**
- **There may be multiple outputs per design**
  - **Solve each output separately**
- **Current approach doesn't have **memory**.**
  - **This will be covered next week.**